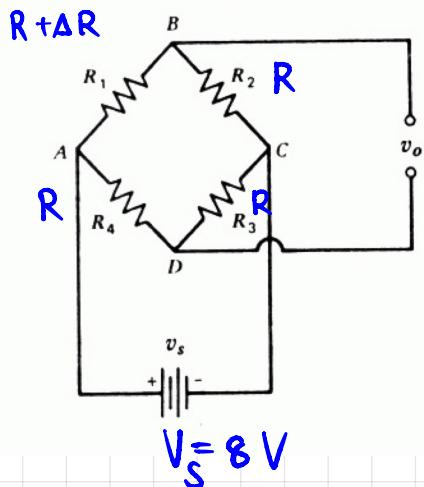


- 6.18 Determine the output voltage v_o as a function of ΔR for the displacement transducer and Wheatstone bridge described in Exercise 6.17 if $v_s = 8 \text{ V}$.



in ex. 6.18 នឹង $R_1 = R_2 = R_3 = R_4 = 1 \text{ k}\Omega$

$$\text{in } v_o = v_{AB} - v_{AD} \quad \text{---(1)}$$

នៅទីនេះ

$$\text{in } v_{AB} = \frac{R_1}{R_1 + R_2} v_s$$

$$\text{ដែល } v_{AB} = \left(\frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2} \right) v_s \quad \text{---(2)}$$

$$\text{នៅ } v_{AD} = \frac{R_4}{R_4 + R_3} v_s \quad \text{---(3)}$$

យើង (2), (3) ទៅ (1) ជា

$$v_o = \left(\frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2} - \frac{R_4}{R_4 + R_3} \right) v_s$$

$$= \left(\frac{1000 + \Delta R_1}{2000 + \Delta R_1} - \frac{1000}{2000} \right) 8$$

$$\therefore v_o = \frac{8000 + 8\Delta R_1}{2000 + \Delta R_1} - 4 \quad \times$$

linearity of the output voltage v_o :

- 6.20 A strain gage with $R_g = 350 \Omega$, $p_T = 0.25 \text{ W}$, and $S_g = 2.05$ is used in arm R_1 of a constant-voltage Wheatstone bridge. If the available power supply is limited to 28 V, determine:
(a) the values of R_2 , R_3 , and R_4 needed to maximize v_o
(b) the circuit sensitivity of the bridge

(a)

in eq. 6.23; $v_s = i_T(R_1 + R_2)$

$$= i_T R_T (1 + r) = (1 + r) \sqrt{p_T R_T}$$

from formula $V_s = 28 \text{ V}$, $p_T = 0.25$, $R_T = R_g = 350$

which is eq. 6.23;

$$28 = (1 + r) \sqrt{(0.25)(350)}$$

$$r = \frac{28}{\sqrt{0.25 \times 350}} - 1$$

$$\therefore r = 1.993$$

in $r = \frac{R_2}{R_1}$ (since $R_1 = R_g = R_T$)

KVL: $R_1 R_3 = R_2 R_4 \rightarrow$

$$\boxed{\frac{R_1}{R_4} = \frac{R_2}{R_3}}$$

from $r = \frac{R_2}{R_1}$

$$1.993 = \frac{R_2}{350}$$

$$\therefore R_2 = 697.55 \Omega$$

Now $R_1 = R_4 = 350 \Omega$, $R_2 = R_3 = 697.55 \Omega$ from eq. 6.15

$$v_o = \frac{R_1 R_3 - R_2 R_4}{(R_1 + R_2)(R_3 + R_4)} v_s \quad \text{in eq. 6.15}$$

$$v_o = \frac{(350)(697.55) - (697.55)(350)}{(350 + 697.55)(697.55 + 350)} \times 28$$

$$\therefore v_o = 0 \text{ V}$$

(b)

$$S_c = \frac{\Delta v_o}{\Delta R_1 / R_1} = \frac{r}{(1 + r)^2} v_s \quad \text{eq. 6.22}$$

$$S_c = \frac{1.993}{(1 + 1.993)^2} (28)$$

$$\therefore S_c = 6.229 \quad \text{X}$$

- 6.29 If we have a common voltage of 0.1 V on the input to a differential amplifier with a gain $G_d = 500$ and we measure a voltage difference $\Delta v = 10$ mV, find the output voltage v_o if the common-mode rejection ratio is as follows:

- (a) 1000 (c) 10,000
 (b) 5000 (d) 20,000

$$v_o = G_d \Delta v + G_c v \quad \text{eq. 6.38.}$$

\nwarrow Common.

, CMRR = $\frac{G_d}{G_c}$

மாதிரி முறை $G_d = 500$, $\Delta V = 10 \text{ mV}$ கால் $V = 0.1 \text{ V}$

@ $G_c = 1000$

$$\therefore V_o = 5.05 \text{ V}$$

$$G_C = 500e$$

$$\therefore V_0 = 500(10 \times 10^{-3}) + \left(\frac{500}{5000}\right)(0.1)$$

$$\therefore V_0 = 5.01 \text{ V}$$

© Gc = 10,000


$$\therefore V_o = 500(10 \times 10^{-3}) + \left(\frac{500}{10,000}\right)(0.1)$$

$$\therefore V_o = 5.005 \text{ V}$$

d $G_C = 200,000$

$$\therefore V_o = 5.0025V$$

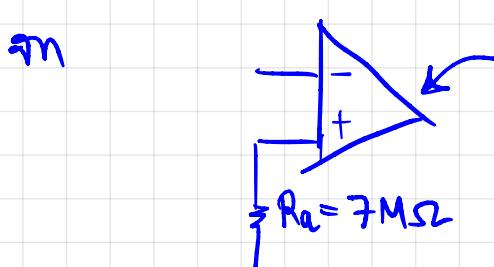- 6.33 Use an op-amp with a gain of 100 dB and $R_a = 7 \text{ M}\Omega$ to design a differential amplifier with a gain of



$$G = 100 \text{ dB}$$

f Ideal

$$\text{Aumento} \frac{R_F}{R_I} = \frac{R_3}{R_2}$$

$$\therefore R_3 = G_C R_2$$


$$\text{រាយការណ៍} \quad R_2 = 7 \text{ M}\Omega$$

a) $G_c = 10$

$$G_C \approx \frac{R_F}{R_1}$$

$$\text{let } R_1 = R_a = 7 \times 10^6 \Omega$$

$$; \quad R_F = 4 \times 10^7 \Omega$$

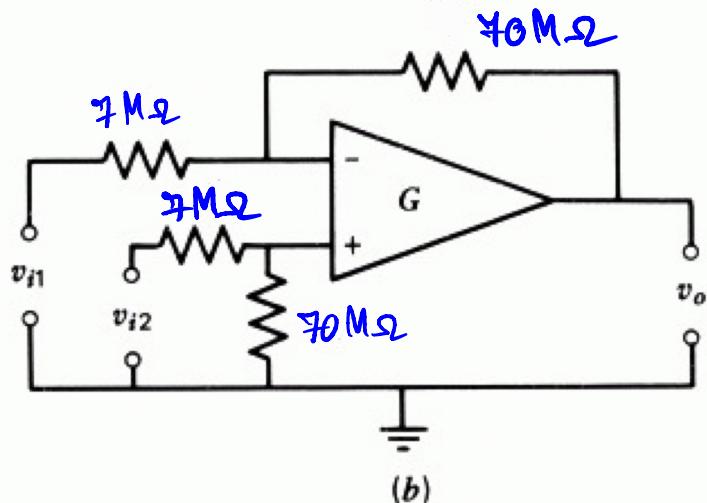


b) $G_C = 20$

గానిస్టస్

$$G_C \approx \frac{R_F}{R_a}$$

$$\therefore R_F = 20 \times 7 \times 10^6$$

$$\therefore R_F = 140 \text{ M}\Omega$$

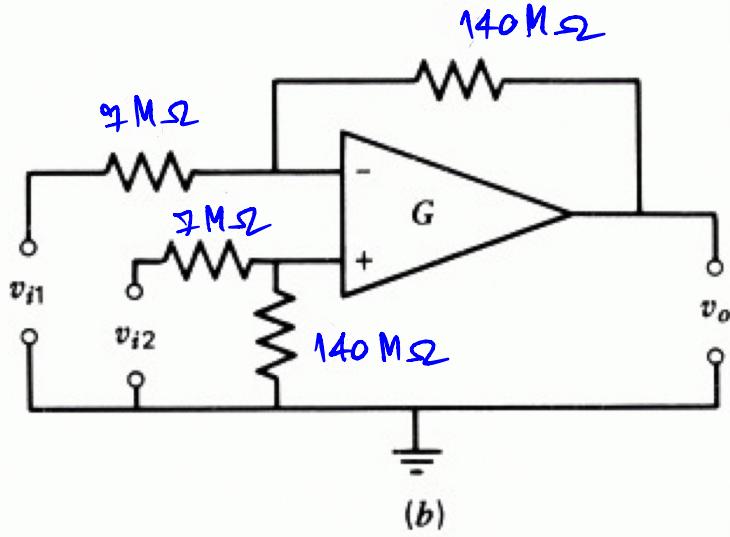


c) $G_C = 50$

గానిస్టస్

$$G_C = \frac{R_F}{R_a}$$

$$\therefore R_F = 50 \times 7 \times 10^6$$

$$\therefore R_F = 350 \text{ M}\Omega$$

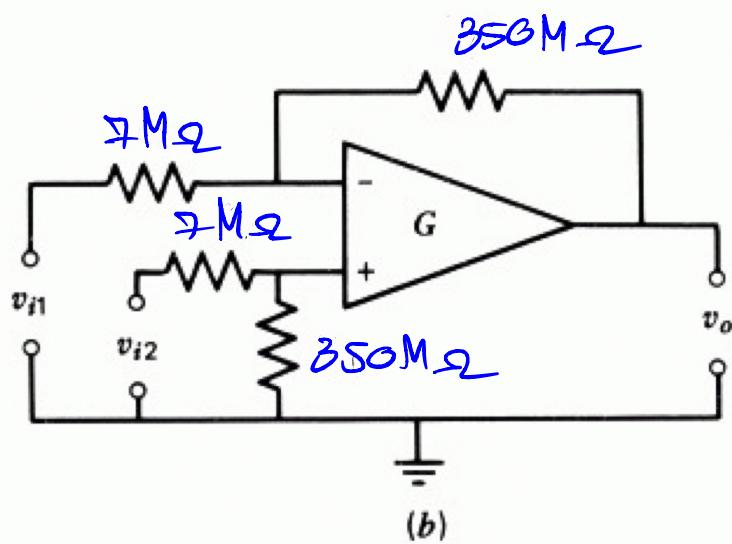


d) $G_C = 100$

గానిస్టస్

$$G_C = \frac{R_F}{R_a}$$

$$\therefore R_F = 10^2 \times 7 \times 10^6$$
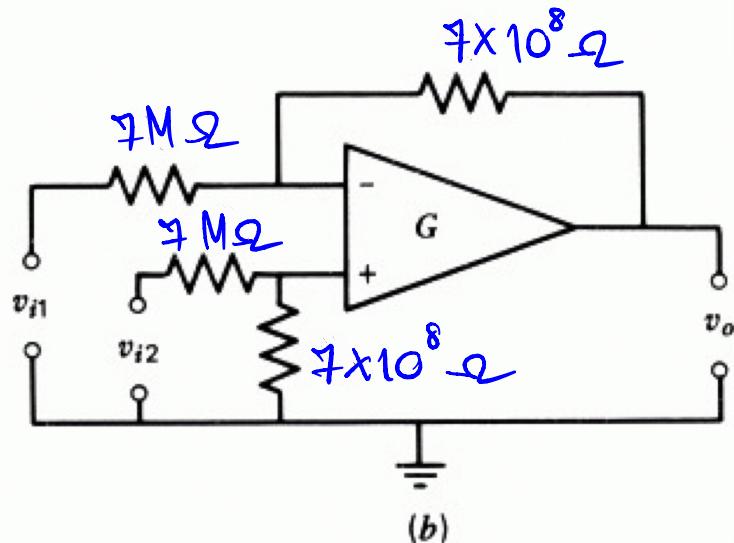
$$\therefore R_F = 7 \times 10^8 \Omega$$



(b) 20 Hz

- 6.47 Select R and C for a low-pass filter that will block 60-Hz noise but transmit the following low-frequency signals with less than 1 percent loss:

(c) 20 Hz

(a) 5 Hz


(b) 10 Hz

... with a critical frequency f_c

$$\text{let } f = 60 \text{ Hz}$$

$$\text{from } \omega = 2\pi f \Rightarrow \omega = 2\pi \times 60$$

$$\therefore \omega = 120\pi$$

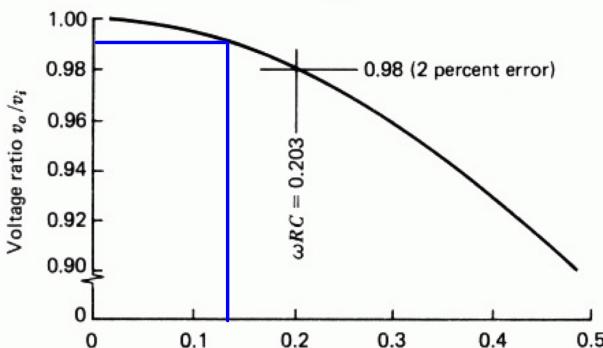

মনে করা ২% এর অর্থাতে
0.98 এর বিরুদ্ধে ১% এর অর্থাতে
অর্থাৎ 0.99 এর বিরুদ্ধে $\omega RC \approx 0.1015$

$$\text{choose } C = 1 \mu\text{F}$$

@ 5 Hz

$$2\pi \times 5 \times R \times 1 \times 10^{-6} = 0.1015$$

$$R = 3230.85 \Omega \quad \text{X}$$

@ 10 Hz

$$2\pi \times 10 \times R \times 1 \times 10^{-6} = 0.1015$$

$$R = 1615.423 \Omega \quad \text{X}$$

@ 20 Hz

$$2\pi \times 20 \times R \times 1 \times 10^{-6} = 0.1015$$

$$R = 807.71 \Omega \quad \text{X}$$