

Homework 3

นายโสมภพ สุขสมบูรณ์

6201011631188 Sec. 3

Elec Measurement (PIV)

- 3.14 The sensitivity of a galvanometer is listed by the manufacturer as $25\text{-}\mu\text{A}$ full scale. The full-scale rotation of the pointer is 45° . Determine the sensitivity S of the galvanometer by using the definition of sensitivity given in Eq. 3.13.

Formula : $\theta = Si$

$$\frac{\pi}{4} = S(25 \times 10^{-6} \text{ A})$$

$$\therefore S = 10,000\pi \text{ rad/A}$$

ดังนั้น ค่า Sensitivity คือ $10,000\pi \text{ rad/A}$ #

- 3.15 A galvanometer with a $40\text{-}\Omega$ coil is rated at 10-mA full scale. Determine the required shunt resistance if it is to be used to measure a current of
- (a) 100 mA (c) 2 A
(b) 0.5 A (d) 20 A

โจทย์กำหนด $i_m = 10 \text{ mA}$, $R_m = 40 \Omega$

Formula : $R_{sh} = \frac{i_m}{i_i - i_m} \times R_m$

(a) $i_i = 100 \text{ mA}$

จ:ได้ $R_{sh} = \frac{10 \times 10^{-3}}{(100 - 10) \times 10^{-3}} \times 40 = 4.445 \Omega$ ✖

(b) $i_i = 0.5 \text{ A}$

จ:ได้ $R_{sh} = \frac{10 \times 10^{-3}}{0.5 - (10 \times 10^{-3})} \times 40 = 0.816 \Omega$ ✖

(c) $i_i = 2 \text{ A}$

จ:ได้ $R_{sh} = \frac{10 \times 10^{-3}}{2 - (10 \times 10^{-3})} \times 40 = 0.201 \Omega$ ✖

(d) $i_i = 20 \text{ A}$

จ:ได้ $R_{sh} = \frac{10 \times 10^{-3}}{20 - (10 \times 10^{-3})} \times 40 = 0.02001 \Omega$ ✖

3.16 Prepare a graph showing the series resistance needed to convert a $50\text{-}\mu\text{A}$ full-scale galvanometer with a coil resistance of $40\ \Omega$ to a multimeter with full-scale voltages that range from 10 mV to 100 V .

formula : $R_{sr} = \frac{V_m^*}{I_m^*} - R_m \Rightarrow$ Terdiketahui
 $- I_m^* = 50 \times 10^{-6}\text{ A}$
 $- R_m = 40\ \Omega$

① $V_m^* = 10\text{ mV}$

; $R_{sr} = \frac{10 \times 10^{-3}}{50 \times 10^{-6}} - 40 = 160\ \Omega$ (0.16, 10)

② $V_m^* = 100\text{ mV}$

; $R_{sr} = \frac{100 \times 10^{-3}}{50 \times 10^{-6}} - 40 = 1960\ \Omega$
 $= 1.96\text{ k}\Omega$ (1.96, 100)

③ $V_m^* = 1\text{ V}$

; $R_{sr} = \frac{1}{50 \times 10^{-6}} - 40 = 19960\ \Omega$
 $= 19.96\text{ k}\Omega$ (19.96, 1000)

④ $V_m^* = 10\text{ V}$

; $R_{sr} = \frac{10}{50 \times 10^{-6}} - 40 = 199,960\ \Omega$
 $= 199.96\text{ k}\Omega$ (199.96, 10000)

⑤ $V_m^* = 100\text{ V}$

; $R_{sr} = \frac{100}{50 \times 10^{-6}} - 40 = 1,999,960\ \Omega$
 $= 1,999.96\text{ k}\Omega$ (1999.96, 100 000)

