

Homework #7

លោកស្រី នាមទុល ស៊ុនិស្សរ៉ាវ 6201011631188

Sec. 3 (PIV)

Measurement

- 7.7 Given 1000 Ω.
Determine the system sensitivity for a bridge with a single active gage having $R_g = 350 \Omega$ and $S_g = 2.05$ if $r = 3$ and if the bridge voltage is 5 V.

$$\text{Forst នៅរដ្ឋ } V_s = (1+r) \sqrt{A P_D R_g} ; \quad P_g = P_D A$$

$$; \quad V_s = (1+r) \sqrt{P_g R_g} \quad \text{--- (1)}$$

$$\text{នៅរដ្ឋ } S_s = \frac{r}{1+r} \frac{S_g \sqrt{P_g R_g}}{r S_g} \quad \text{--- (2)}$$

$$\sqrt{P_g R_g} = \frac{S_s (1+r)}{r S_g} \quad \text{--- (2)}$$

ឱ្យ (2) ធ្វើ (1) ;

$$V_s = \frac{(1+r)^2}{r S_g} S_s$$

$$; \quad S_s = \frac{r V_s S_g}{(1+r)^2} \quad \text{--- (3)}$$

ឱ្យ (3) $V_s = 5$, $r = 3$, $S_g = 2.05$ ធ្វើ (3) ;

$$S_s = \frac{3(5)(2.05)}{(1+3)^2}$$

$$\therefore S_s = 1.921845 \Omega/V \quad \times$$

- 7.9 Determine the voltage output from a Wheatstone bridge if a single active gage is used in an initially balanced bridge to measure a strain of 1200 $\mu\text{m/m}$. Assume that a digital voltmeter will be used to measure the voltage and that $S_e = 2.06$, $r = 1$, and $V_s = 6 \text{ V}$.

$$\text{នៅរដ្ឋ } V_s = (1+r) \sqrt{P_g R_g} \quad \text{--- (1)}$$

$$; \quad S_s = \frac{r S_g \sqrt{P_g R_g}}{1+r} \quad \text{--- (2)}$$

$$\text{នៅរដ្ឋ } \frac{\Delta V_o}{\epsilon} = S_s \Rightarrow \Delta V_o = \epsilon S_s \quad \text{--- (3)}$$

$$\text{ឱ្យ (3) ធ្វើ (2); } \Delta V_o = \frac{\epsilon r S_g \sqrt{P_g R_g}}{1+r} \quad \text{--- (4)}$$

$$\sqrt{P_g R_g} = \frac{\Delta V_o (1+r)}{S_g \epsilon r} \quad \text{--- (5)}$$

ឱ្យ (5) ធ្វើ (1) ;

$$V_s = (1+r) \Delta V_o \frac{(1+r)}{\epsilon r S_g}$$

$$; \quad \Delta V_o = \frac{\epsilon V_s r S_g}{(1+r)^2} \quad \text{--- (6)}$$

ឱ្យ (6) ;

$$\Delta V_o = \frac{1200 \mu \times 6 \times 1 \times 2.06}{(1+1)^2}$$

$$= 3.708 \text{ mV} \quad \times$$

- 7.11 A 350- Ω strain gage with $S_g = 2.07$ is employed in a single-arm Wheatstone bridge with $r = 1$. If the gage is subjected to a strain of 1600 $\mu\text{in./in.}$, determine the reading on a $4\frac{1}{2}$ -digit DVM if

v_s (V)	Amplifier Gain G
(a) 2	10
(b) 4	10
(c) 6	100
(d) 5	50

$$v_s = (1 + r) \sqrt{p_g R_g} \quad \text{---(1)} \quad \Delta v_o = \frac{r}{1 + r} \sqrt{p_g R_g} S_g \epsilon \quad \text{---(2)}$$

$$\text{from (2); } \sqrt{p_g R_g} = \frac{\Delta v_o (1+r)}{r S_g \epsilon} \quad \text{---(3)} \quad \text{from (1);}$$

$$v_s = \frac{(1+r) \Delta v_o}{r S_g \epsilon} \Rightarrow \Delta v_o = \frac{r S_g \epsilon v_s}{(1+r)^2} \quad \text{---(4)}$$

(a) $v_s = 2\text{ V}, G = 10$

$$\text{from (4); } \Delta v_o = \frac{1 \times 2.07 \times 1600 \times 10^{-6} \times 2}{(1+1)^2}$$

$$\Delta v_o = 1.656 \text{ mV}$$

then $G = 10 ; \Delta v_o = 1.656 \text{ mV} = 0.01656 \text{ V}$

 $\text{from (4) } 0.016 \text{ V}$ 
 $4\frac{1}{2}$

(b) $v_s = 4, G = 10$

$$\text{from (4); } \Delta v_o = \frac{1 \times 2.07 \times 1600 \times 10^{-6} \times 4}{(1+1)^2}$$

$$\Delta v_o = 3.312 \text{ mV}$$

then $G = 10 ; \Delta v_o = 3.312 \text{ mV} = 0.03312 \text{ V}$

 $\text{from (4) } 0.033 \text{ V}$ 
 $4\frac{1}{2}$

- 7.11 A $350\text{-}\Omega$ strain gage with $S_g = 2.07$ is employed in a single-arm Wheatstone bridge with $r = 1$. If the gage is subjected to a strain of $1600 \mu\text{in./in.}$, determine the reading on a $4\frac{1}{2}$ -digit DVM if

	v_s (V)	Amplifier Gain G
(a)	2	10
(b)	4	10
(c)	6	100
(d)	5	50

(c) $V_s = 6V \quad G = 100$

இழுதிடல் (4); $\Delta V_o = \frac{1 \times 2.07 \times 1600 \times 10^{-6} \times 6}{(1+1)^2}$

$\therefore \Delta V_o = 4.968 \text{ mV}$

மு $G = 100$; $\Delta V_o = 496.8 \text{ mV} = 0.4968 \text{ V}$

18.0000
4 1/2

ஏதோயிர்கீ 0.496 V

X

(d) $V_s = 5V, \quad G = 50$

இழுதிடல் (4); $\Delta V_o = \frac{1 \times 2.07 \times 1600 \times 10^{-6} \times 5}{(1+1)^2}$

$\therefore \Delta V_o = 4.14 \text{ mV}$

மு $G = 50$; $\Delta V_o = 207 \text{ mV} = 0.207 \text{ V}$

ஏதோயிர்கீ 0.207 V

X

18.0000

- 7.13 Four strain gages ($R_g = 500 \Omega$, $S_g = 2.06$) are attached to a bar to produce a load cell. The supply voltage $v_s = 4 \text{ V}$ and the amplifier (with a variable gain 10–100) is set at $G = 20$. When a load of 10,000 lb is applied to the bar the $4\frac{1}{2}$ -digit DVM provides a count of 6280. What adjustments are required to make the count correspond to the applied load?

Ans

$$\Delta V_o = \frac{10000 \mu - 6280 \mu}{20} = 0.186 \text{ mV} \quad \left| \begin{array}{l} 0.186 \text{ mV} = 4 \frac{\Delta R_g}{500} \\ \Delta R_g = 23.25 \text{ M}\Omega \end{array} \right. \times$$

- 7.14 An oscilloscope with an input impedance of $10^6 \Omega$ is connected to a Wheatstone bridge with one active gage ($R_g = 350 \Omega$, $S_g = 3.35$, and $r = 5$). The bridge is powered with a 9-V constant-voltage supply. If the gage responds to a dynamic strain pulse having a magnitude of $900 \mu\text{m/m}$, determine the sensitivity setting on the oscilloscope that will give a trace deflection of four divisions.

Ans

$$S_R d_s = \frac{r}{(1+r)^2} v_s S_g \epsilon$$

$$S_R (4) = \frac{5}{(1+5)^2} \times 9 \times 3.35 \times 900 \times 10^{-6}$$

$$S_R = 942.1875 \mu\text{V/DIV} \times$$