

Homework #4

ນາຍໂສດຖຸ ສູງສວນບູກໄນ້ 6201011637788 SEC. 3 (P I V)

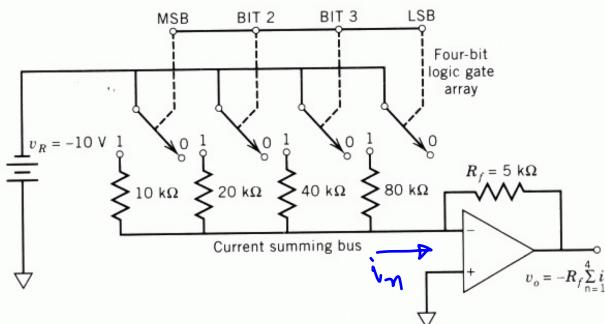


Figure 4.5 Schematic diagram of a simple 4-bit digital-to-analog converter.

(a) 1101

$$\text{let } i_n = \frac{V_R}{R_n}; n=1,2,3,4; V_R = -10V$$

$$i_1 = -\frac{10}{10k} = -1 \times 10^{-3} A = -1 \text{ mA}$$

$$i_2 = -\frac{10}{20k} = -0.5 \times 10^{-3} A = -0.5 \text{ mA}$$

$$\text{formula: } \theta_0 = -R_f \sum_{n=1}^4 i_n$$

$$\begin{aligned} \Theta_0 &= (-5k) \sum_{n=4}^4 i_n \\ &= (-5k) [-1m - 0.5m + 0 - 0.125m] \\ &= \cancel{(-5k)} \left[\cancel{-1.625m} \right] \end{aligned}$$

$$\therefore V_0 = 8.125 \text{ V} \quad \cancel{\text{X}}$$

4.13 For the 4-bit DAC shown in Fig. 4.5, determine the output voltage v_o for the following digital codes:

- | | | |
|----------|----------|----------|
| (a) 1101 | (c) 0110 | (e) 1001 |
| (b) 1010 | (d) 0101 | (f) 1110 |

c) 1010

$$i_1 = -\frac{10}{10k} = -1 \times 10^{-3} A = -1 \text{ mA}$$

$$i_2 = i_4 = 0 \text{ mA}$$

$$i_3 = -\frac{10}{40k} = -0.25 \text{ mA}$$

$$\text{ຈິກ } \quad \vartheta_0 = (-5k) [-1m - 0.25m] \\ = (-5k)(-1.25m)$$

CC 0110

$$i_1 = i_4 = 0 \text{ mA}$$

$$i_2 = -\frac{10}{20k} = -0.5 \text{ mA}$$

$$i_3 = \frac{-10}{40k} = -0.25 \text{ mA}$$

$$7.16 \quad V_o = (-5k) [-0.5m - 0.25m] \\ = (-5k) [-0.75m]$$

$$\therefore V_0 = 3.75 \text{ V} \cancel{\times}$$

- 4.13 For the 4-bit DAC shown in Fig. 4.5, determine the output voltage v_o for the following digital codes:

(a) 1101
(b) 1010

(c) 0110
(d) 0101

(e) 1001
(f) 1110

(d) 0101

$$i_1 = i_3 = 0 \text{ mA}$$

$$i_2 = -\frac{10}{20k} = -0.5 \text{ mA}$$

$$i_4 = -\frac{10}{80k} = -0.125 \text{ mA}$$

∴ $v_o = (-5k) [-0.5 - 0.125] \text{ mV}$

$$\therefore v_o = 0.125 \text{ V} \times \cancel{\text{X}}$$

(e) 1001

$$i_1 = -\frac{10}{10k} = -1 \text{ mA}$$

$$i_2 = i_3 = 0 \text{ mA}$$

$$i_4 = -\frac{10}{80k} = -0.125 \text{ mA}$$

∴ $v_o = (-5k) [-1 - 0.125] \text{ mV}$

$$\therefore v_o = 5.625 \text{ V} \times \cancel{\text{X}}$$

(f) 1110

$$i_1 = -\frac{10}{10k} = -1 \text{ mA}$$

$$i_2 = -\frac{10}{20k} = -0.5 \text{ mA}$$

$$i_3 = -\frac{10}{40k} = -0.25 \text{ mA}$$

$$i_4 = 0 \text{ mA}$$

∴ $v_o = (-5k) [-1 - 0.5 - 0.25] \text{ mV}$

$$\therefore v_o = 8.75 \text{ V} \times \cancel{\text{X}}$$

- 4.17 Prepare an illustration, similar to Fig. 4.7, that demonstrates A/D conversion by the method of successive approximations if the fixed analog input voltage v_u is

(a) 1/8 FSV
(b) 7/16 FSV
(c) 3/4 FSV
(d) 13/16 FSV

let $n = 4$ (number of Digits)

ສຳເນົານິຕີສອບລະກົດເປົ້າ 0010




(a) 1/8 FSV

$$; v_b = \frac{1}{8} \text{ FSV} + \frac{1}{2^5} \text{ FSV} = \frac{5}{32} \text{ FSV} = \frac{2.5}{16} \text{ FSV}$$

formula: $v_b = v_u + \frac{1}{2^{n+1}} \text{ FSV}$

Register	D/A FSV	comparator
1000	8/16	$v_o > v_b$
0100	4/16	$v_o > v_b$
0010	2/16	$v_o < v_b$
0011	3/16	$v_o > v_b$
0010	2/16	$v_o < v_b$
0100	4/16	$v_o > v_b$

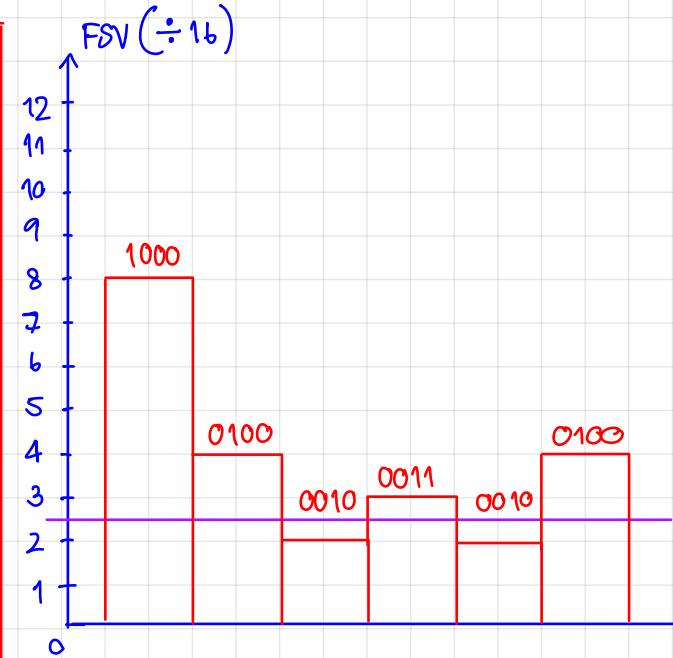

- 4.17 Prepare an illustration, similar to Fig. 4.7, that demonstrates A/D conversion by the method of successive approximations if the fixed analog input voltage v_u is


- (a) 1/8 FSV (c) 3/4 FSV
 (b) 7/16 FSV (d) 13/16 FSV

Formula: $v_b = v_u + \frac{1}{2^{n+1}} \text{FSV}$

c) 7/16 FSV

$$\text{Then } v_b = v_u + \frac{1}{2^{n+1}} \text{FSV} ; v_b = \frac{7}{16} \text{FSV} + \frac{1}{2^5} \text{FSV} \\ = \frac{15}{32} \text{FSV} = \frac{7.5}{16} \text{FSV}$$

Register	D/A FSV	comparator
1000	8/16	$v_o > v_b$
0100	4/16	$v_o < v_b$
0110	6/16	$v_o < v_b$
0111	7/16	$v_o < v_b$
1000	8/16	$v_o > v_b$
0111	7/16	$v_o < v_b$

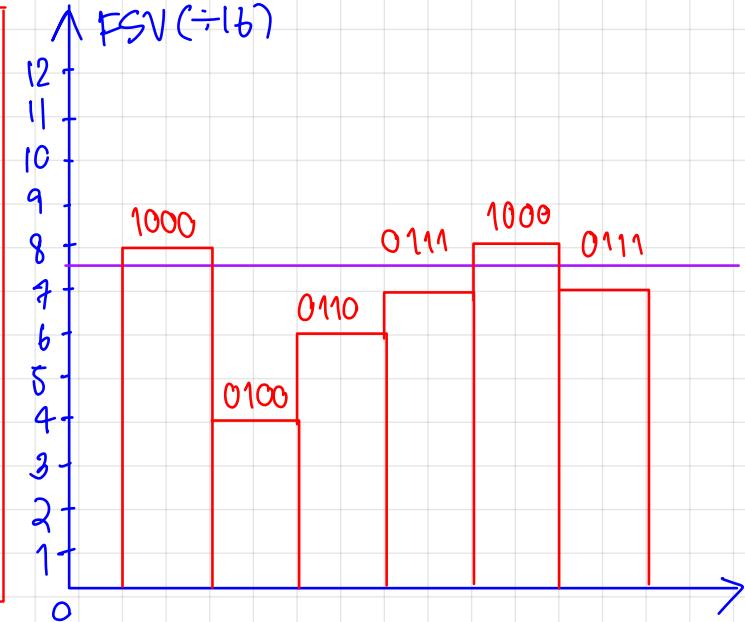


ต้องห้ามค่า 0111 ไม่ได้คือ 0111 ✗

(c) 3/4 FSV

$$\text{Then } v_b = v_u + \frac{1}{2^{n+1}} \text{FSV} ; v_b = \frac{3}{4} \text{FSV} + \frac{1}{32} \text{FSV} = \frac{25}{32} \text{FSV} = \frac{12.5}{16} \text{FSV}$$

Register	D/A FSV	Comparator
1000	8/16	$v_o < v_b$
1100	12/16	$v_o < v_b$
1110	14/16	$v_o > v_b$
1100	12/16	$v_o < v_b$

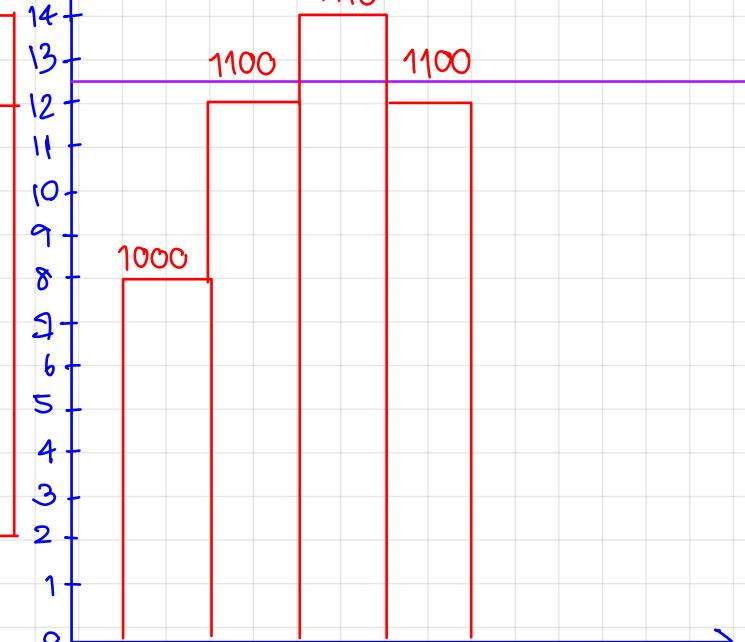

ต้องห้ามค่า 0111 ไม่ได้คือ 1100 ✗


- 4.17 Prepare an illustration, similar to Fig. 4.7, that demonstrates A/D conversion by the method of successive approximations if the fixed analog input voltage v_u is

- (a) 1/8 FSV (c) 3/4 FSV
 (b) 7/16 FSV (d) 13/16 FSV

(d) 13/16 FSV

$$\text{an } v_b = v_{ut} + \frac{1}{2^{n+1}} \text{ FSV} ; v_b = \frac{13}{16} \text{ FSV} + \frac{1}{2^{n+1}} \text{ FSV} = \frac{27}{32} \text{ FSV} = \frac{13.5}{32} \text{ FSV}$$

Register	D/A FSV	comparator
1000	8/16	$v_o < v_b$
1100	12/16	$v_o < v_b$
1110	14/16	$v_o > v_b$
1100	12/16	$v_o < v_b$
1101	13/16	$v_o < v_b$
1110	14/16	$v_o > v_b$
1101	13/16	$v_o < v_b$

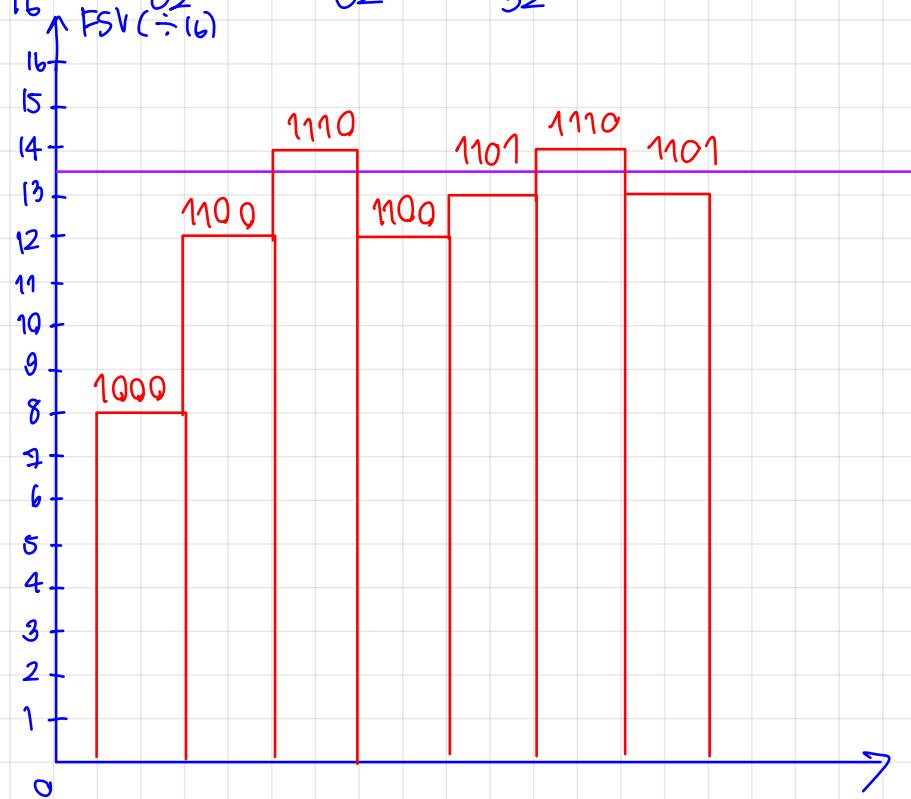

តើវិនិច្ឆ័យទី២ តើ 1101 ✗

- 4.23 Verify Eq. 4.16 beginning with ω_1 .
 4.24 Determine the frequency limit of a 12-bit unipolar dual-slope integrating A/D converter capable of 20 readings per second.

Formula : $f < \frac{2^{-n}}{\pi T}$

$$\text{an } f < \frac{2^{-n}}{\pi T} \quad \text{ការងារបាន} \quad n = 12\text{-bit} \quad \text{នៃ: } f = 20 \text{ s}^{-1}$$

$$; \quad f < \frac{2^{-12}}{\pi \left(\frac{1}{10} \right)}$$

$$f < \frac{10 \times 2^{-12}}{\pi} = 0.777 \times 10^{-3} \text{ Hz}$$

$$\therefore f < 0.777 \text{ mHz}$$

$$f = \frac{1}{T}$$

* Nominal Dual-slope

$$f = \frac{2}{T}$$

- 4.25 Determine the frequency limit in Hz.
 4.26 Determine the slew rate of the A/D converter in Exercise 4.24 if the FSV is

(a) 1 V (b) 2 V	(c) 5 V (d) 10 V
--------------------	---------------------

$$\text{From eq. 4.14; } \left(\frac{dv_u}{dt} \right)_{\max} = \pi f v_u^*$$

The term $(dv_u/dt)_{\max}$ is called the slew rate of the signal.

$$\text{从图 A.24 看到 } f = 0.777 \text{ MHz}$$

$$\text{则 } f = 10 \times 2^{-12} \frac{\text{Hz}}{\pi}$$

(a) 1 V

$$\left(\frac{d}{dt} V_u \right)_{\max} = \pi f^* v_u^*$$

$$; \quad \left(\frac{dV_u}{dt} \right)_{\max} = \cancel{\pi x} \left(\frac{10 \times 2}{\cancel{\pi}} \right)^{-12} s^{-1} \times 1 \text{ V}$$

$$\therefore \left(\frac{d(V_a)}{dt} \right)_{\text{max}} = 2.441 \text{ mV/s}$$

(b) 2 ✓

$$\text{From eq. 4.14; } \left(\frac{dV_u}{dt} \right)_{\max} = \pi \times \frac{10 \times 2}{\pi}^{-12} \text{ s}^{-1} \times 2 \text{ V}$$

$$\therefore \left(\frac{dV_u}{dt} \right)_{\max} = 4.882 \text{ mV/s}$$

(c) 5 V

$$\text{In eq. 4.14 j } \left(\frac{dv_u}{dt} \right)_{\max} = \pi \times \frac{10 \times 2}{\pi}^{-12} s^{-1} \times 5 V$$

$$\therefore \left(\frac{dV_u}{dt} \right)_{\max} = 12.207 \text{ mV/s}$$

(d) 10 V

$$\text{from eq. 4.14; } \left(\frac{dV_U}{dt} \right)_{\max} = \pi \times \frac{10 \times 2}{\pi}^{-12} \text{ s}^{-1} \times 10V$$

$$\therefore \left(\frac{dV_H}{dt} \right)_{\max} = 24.414 \text{ mV/s} \quad \cancel{\text{X}}$$

- 4.40 You are to measure a voltage v_i with a $5\frac{1}{2}$ -digit DVM capable of 100% over-ranging. If the meter is specified with an accuracy of $\pm 0.002\%$ and ± 2 counts, determine the maximum and minimum readings anticipated if v_i is

- (a) 1.80000 V (b) 2.50000 V (c) 9.99996 V

$$\text{Measurement Error} = \pm (0.002\% \cdot \text{rdg} + 2d)$$

(a) 1.80000 V

$\Rightarrow 5\frac{1}{2} \text{ Digit}$

$\Rightarrow d=5 \text{ digits.}$

$$\text{Measurement Error} = \pm (0.002\% \cdot \text{rdg} + 2d)$$

$$; \text{ Measurement Error} = \pm (0.002\% \cdot (1.80000) + 2(0.0001))$$

$$= \pm 5.6 \times 10^{-5} \text{ V}$$

∴ Maximum readings anticipated is $1.80000 \text{ V} + 5.6 \times 10^{-5} \text{ V} = 1.800056 \text{ V}$

Minimum readings anticipated is $1.80000 \text{ V} - 5.6 \times 10^{-5} \text{ V} = 1.799944 \text{ V}$

X

(b) 2.50000 V

$\Rightarrow d=4 \text{ digits.}$

X

$$\text{Measurement Error} = \pm (0.002\% \cdot \text{rdg} + 2d)$$

$$; \text{ Measurement Error} = \pm (0.002\% \cdot (2.50000) + 2(0.0001))$$

$$= \pm 0.25 \times 10^{-3} \text{ V}$$

∴ Maximum readings anticipated is $2.50000 + 0.25 \times 10^{-3} = 2.50025 \text{ V}$

Minimum readings anticipated is $2.50000 - 0.25 \times 10^{-3} = 2.49975 \text{ V}$

X

(c) 9.99996 V

$\Rightarrow d=4 \text{ digits}$

X

$$\text{Measurement Error} = \pm (0.002\% \cdot \text{rdg} + 2d)$$

$$; \text{ Measurement Error} = \pm (0.002\% \cdot (9.99996) + 2(0.0001))$$

$$= \pm 3.999 \times 10^{-4} \text{ V}$$

∴ Maximum readings anticipated is $9.99996 + 3.999 \times 10^{-4} = 10.00036 \text{ V}$

Minimum readings anticipated is $9.99996 - 3.999 \times 10^{-4} = 9.99956 \text{ V}$

X